

IMPLEMENTATION OF SEQUENCE DETECTOR USING LED IN ARDUINO

Pavan NagaSurya Cheemalamarry
 pavannagasuryach18.555@gmail.com
 IITH - Future Wireless Communication (FWC22137)

CONTENTS

I	Question	1
II	Answer	1
	II-A Truth Table	1
	II-B K-Map Implementation of y	1
	II-C K-Map Implementation of $D1$	2
	II-D K-Map Implementation of $D2$	2
III	Components	2
IV	Implementation	2

A. Truth Table

p	q	x	\bar{p}	\bar{q}	y	$D1$	$D2$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	1	0	0	1
1	0	0	0	0	0	0	0
1	0	1	0	1	1	0	1
1	1	0	x	x	x	x	x
1	1	1	x	x	x	x	x

Truth table for Boolean function


I. QUESTION

A sequence detector is designed to detect precisely 3 digital inputs, with overlapping sequence detectable. For the sequence (1, 0, 1) and input data (1, 1, 0, 1, 0, 0, 1, 1, 0, 1, 0, 1, 1, 0)

- 1) 1,1,0,0,0,0,1,1,0,1,0,0
- 2) 0,1,0,0,0,0,0,1,0,1,0,0
- 3) 0,1,0,0,0,0,0,1,0,1,1,0
- 4) 0,1,0,0,0,0,0,1,0,1,0,0

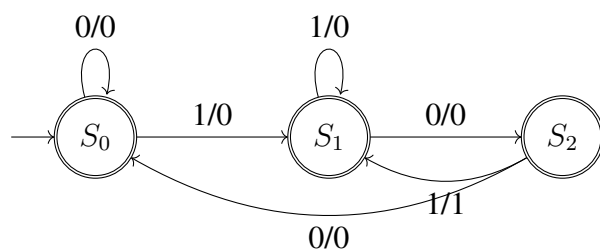II. ANSWER

The above question can be solved by using State diagram, Truth Table and karnaugh-map.



B. K-Map Implementation of y

		qx			
		00	01	11	10
p	0	0	0	0	0
	1	0	1	X	X

Table. 1

herefore, the Boolean function is $y = px$.

C. K-Map Implementation of D1

		qx			
		00	01	11	10
p	0	0	0	0	1
	1	0	0	X	X

Table. 2

Therefore, the Boolean function is $D1 = q\bar{x}$.

D. K-Map Implementation of D2

		qx			
		00	01	11	10
p	0	0	1	1	0
	1	0	1	X	X

Table. 3

Therefore, the Boolean function is $D2 = x$.

III. COMPONENTS

Components	Values	Quantity
Arduino	Uno	1
Jumper Wires	M-M	7
Breadboard		1
LED		2
Resistor	220 ohms	2

IV. IMPLEMENTATION

Arduino PIN	INPUT	OUTPUT
2	manual	
3		LED
13		LED

Procedure

1. Connect the circuit as per the above table.
2. Upload the code for arduino from the below link.

<https://github.com/pavannagasuryach/cbse-12th-optimization/tree/main/IDE/ARM>

3. Change the values of **Inputs** in the Hardware and verify the sequence.