

IMPLEMENTATION OF SEQUENCE DETECTOR USING LED IN ARDUINO

Pavan NagaSurya Cheemalamarry
 pavannagasuryach18.555@gmail.com
 IITH - Future Wireless Communication (FWC22137)

CONTENTS

| | | |
|------------|-----------------------------------|---|
| I | Question | 1 |
| II | Answer | 1 |
| | II-A Truth Table | 1 |
| | II-B K-Map Implementation of y | 1 |
| | II-C K-Map Implementation of $D1$ | 1 |
| | II-D K-Map Implementation of $D2$ | 2 |
| III | Components | 2 |
| IV | Implementation | 2 |

A. Truth Table

| p | q | x | \bar{p} | \bar{q} | y | $D1$ | $D2$ |
|-----|-----|-----|-----------|-----------|-----|------|------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | x | x | x | x | x |
| 1 | 1 | 1 | x | x | x | x | x |

Truth table for Boolean function


I. QUESTION

A sequence detector is designed to detect precisely 3 digital inputs, with overlapping sequence detectable. For the sequence $(1, 0, 1)$ and input data $(1, 1, 0, 1, 0, 0, 1, 1, 0, 1, 0, 1, 1, 0)$

- 1) 1,1,0,0,0,0,1,1,0,1,0,0
- 2) 0,1,0,0,0,0,0,1,0,1,0,0
- 3) 0,1,0,0,0,0,0,1,0,1,1,0
- 4) 0,1,0,0,0,0,0,1,0,1,0,0

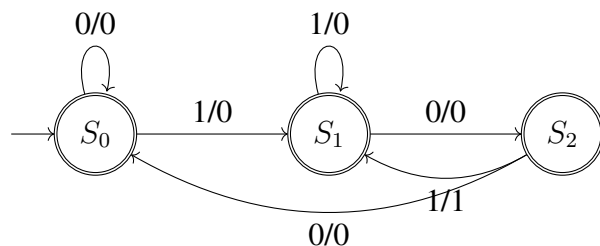II. ANSWER

The above question can be solved by using State diagram, Truth Table and karnaugh-map.



B. K-Map Implementation of y

| | | | | | |
|-----|---|------|----|----|----|
| | | qx | | | |
| | | 00 | 01 | 11 | 10 |
| p | 0 | 0 | 0 | 0 | 0 |
| | 1 | 0 | 1 | X | X |

Table. 1

herefore, the Boolean function is $y = px$.

C. K-Map Implementation of D1

| | | | | | |
|-----|---|------|----|----|----|
| | | qx | | | |
| | | 00 | 01 | 11 | 10 |
| p | 0 | 0 | 0 | 0 | 1 |
| | 1 | 0 | 0 | X | X |

Table. 2

Therefore, the Boolean function is $D1 = q\bar{x}$.

D. K-Map Implementation of D2

| | | | | | |
|-----|---|------|----|----|----|
| | | qx | | | |
| | | 00 | 01 | 11 | 10 |
| p | 0 | 0 | 1 | 1 | 0 |
| | 1 | 0 | 1 | X | X |

Table. 3

Therefore, the Boolean function is $D2 = x$.

III. COMPONENTS

| Components | Values | Quantity |
|--------------|----------|----------|
| Arduino | Uno | 1 |
| Jumper Wires | M-M | 7 |
| Breadboard | | 1 |
| LED | | 2 |
| Resistor | 220 ohms | 2 |

IV. IMPLEMENTATION

| Arduino PIN | INPUT | OUTPUT |
|-------------|--------|--------|
| 2 | manual | |
| 3 | | LED |
| 13 | | LED |

Procedure

1. Connect the circuit as per the above table.
2. Upload the code for arduino from the below link.

<https://github.com/pavannagasuryach/cbse-12th-optimization/tree/main>

3. Change the values of **Inputs** in the Hardware and verify the sequence.